



SHORT NOTES

C H A P T E R

Electric Power



+91 999021287




www.visualphysics.in



ELECTRIC POWER

heating effect \rightarrow when current pass through a conductor it becomes hot.

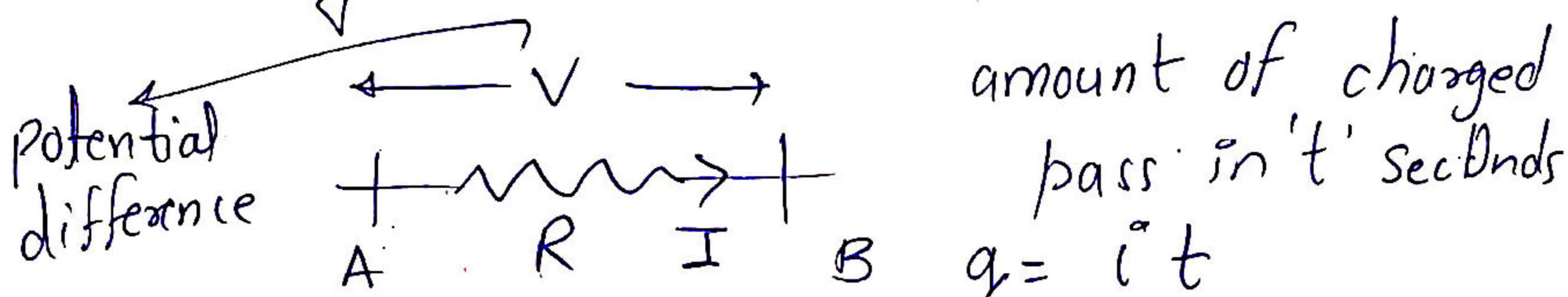↓
due to collisions of drifting electrons inside the conductor, loss of electrons k.E results in heating of conductor.



$$\text{loss in potential energy} = qV = iVt$$

$$\text{as } V = iR$$

$$\Rightarrow \boxed{\text{Energy loss} = i^2 R t}$$

$$\text{or Energy loss} = \frac{V^2}{R} t$$

So in terms of energy loss per seconds

$$\text{i.e. } \boxed{\text{power loss} = i^2 R = \frac{V^2}{R}}$$

Joules law of heating,

$$\begin{array}{l} \text{Heat produced} \propto i^2 \\ \propto t \\ \propto R \end{array} \quad \left| \quad \Rightarrow \text{heat lost} = \underline{i^2 R t} \right.$$

$$1 \text{ cal} = 4.18 \text{ J} = 4.2 \text{ J}$$

$$1 \text{ kWh} = 1000 \text{ W} \times \text{hour} = 1000 \text{ W} \times 3600 \text{ s} \\ = 3.6 \times 10^6 \text{ J}$$

1 kWh \rightarrow power consumed 1 kW for one hour

$$1 \text{ hp} = 746 \text{ W}$$

\rightarrow In series \rightarrow as current is same in series


$$P = I^2 R, \text{ more } R \text{ more Power loss}$$

\rightarrow In parallel:

$$P = \frac{V^2}{R}, \text{ less } R, \text{ more power loss.}$$

as resistors have same potential difference in parallel.

Maximum power Transfer

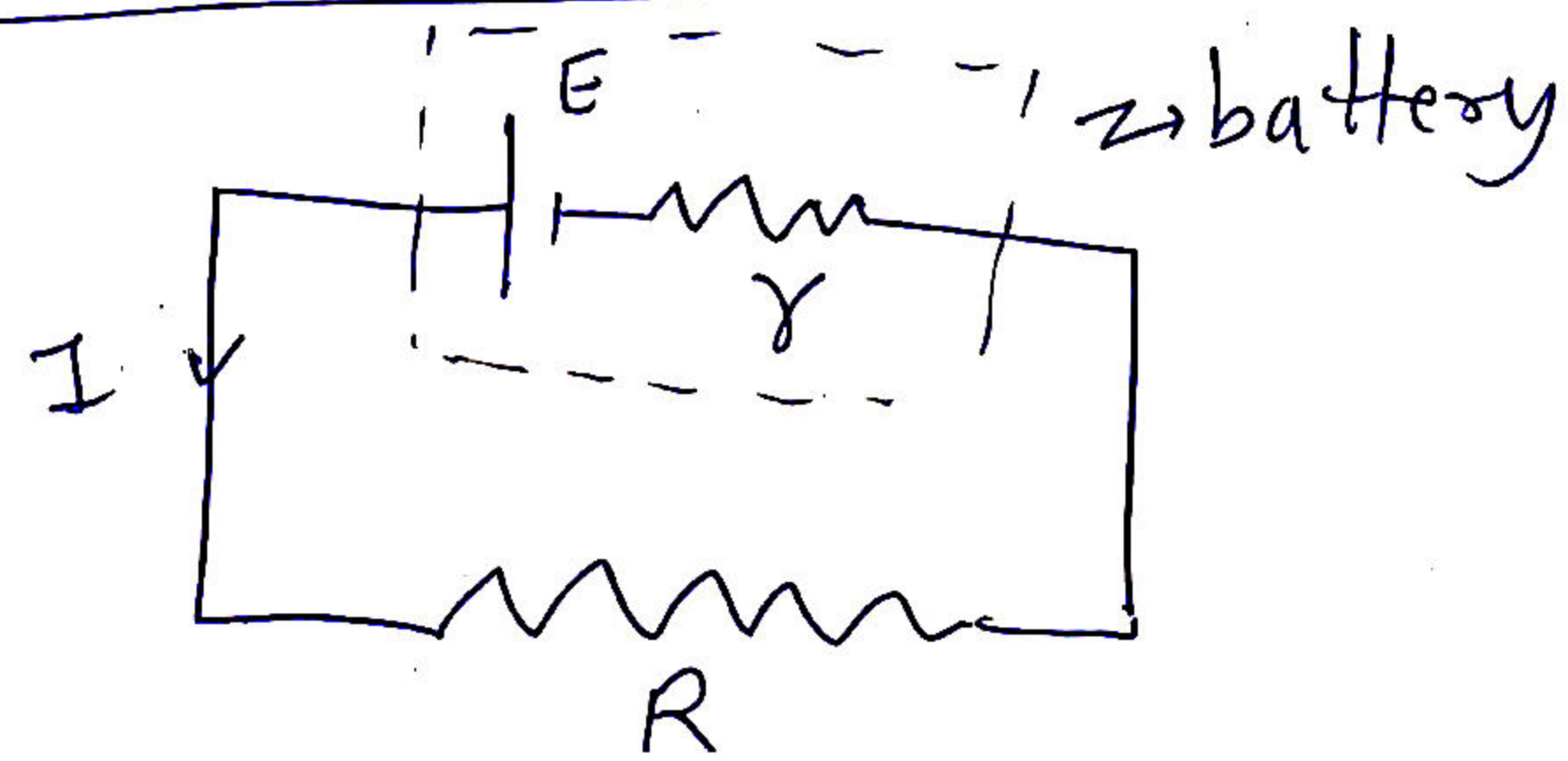

As power loss in external resistor = $I^2 R$

$$I = \frac{E \xrightarrow{\text{emf}}}{R+r}$$

$$P = \frac{E^2 R}{(R+r)^2}$$

$$\frac{dP}{dR} = 0, \quad E^2 \left[\frac{(R+r)^2 - 2(R)(R+r)}{(R+r)^4} \right] = 0$$

$$\Rightarrow (r+R) = 2R \quad \text{or} \quad \boxed{r=R}$$


So if external resistance = internal resistance
then maximum power output to external
system R.

Electric Appliances :

Each Appliance requires power

↳ Rating $[P_0, V_0]$ $\xrightarrow{\text{Rated power}}$
 $\xrightarrow{\text{Rated voltage}}$

that means:

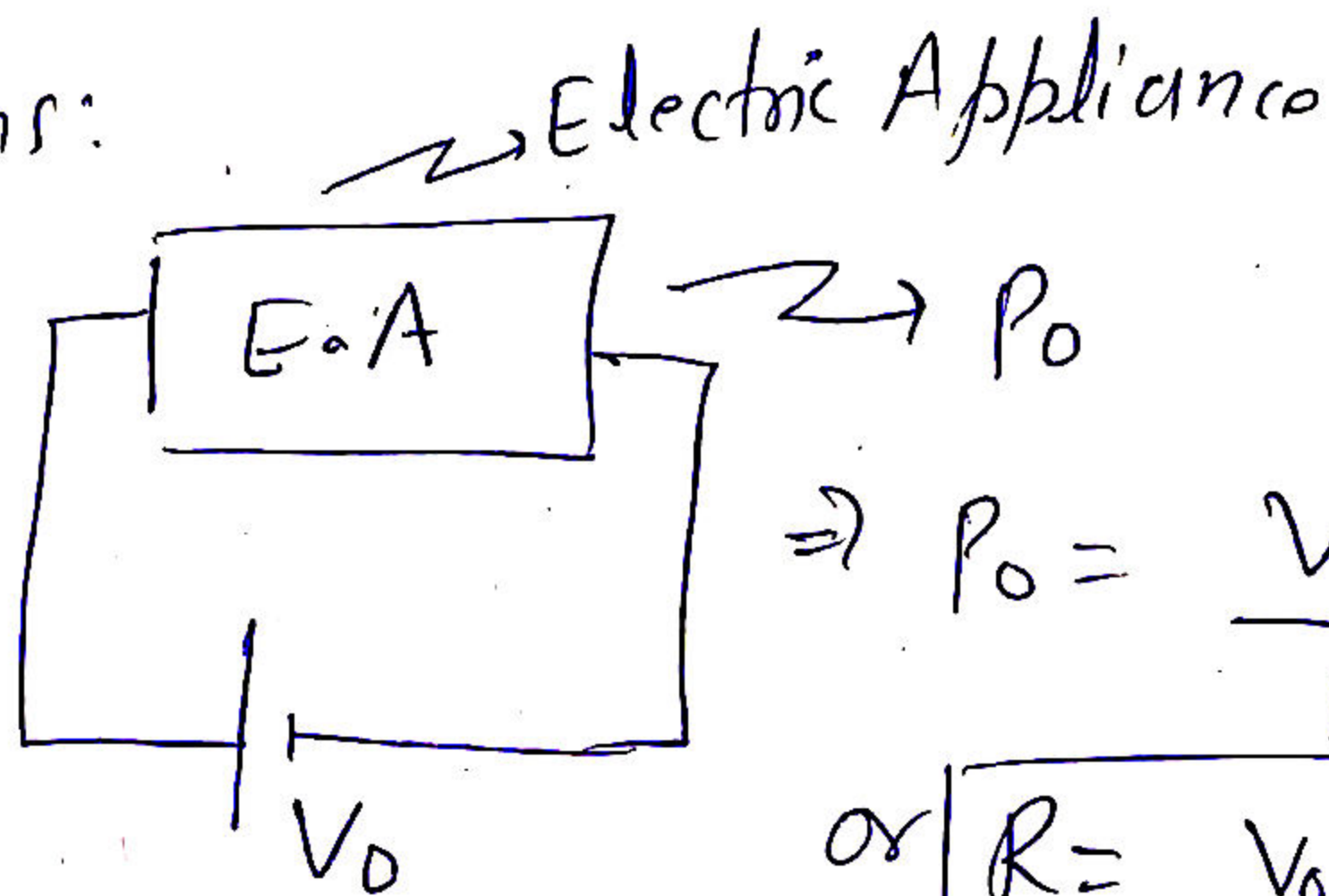

$$\Rightarrow P_0 = \frac{V_0^2}{R}$$

$$\text{or } R = \frac{V_0^2}{P_0}$$

if power supplied by V

$$\Rightarrow P = \frac{V^2}{R} = \frac{V^2}{V_0^2} P_0$$

$$\Rightarrow P = \left(\frac{V}{V_0}\right)^2 P_0$$

↘ as appliance work on specific maximum current.

if $V > V_0 \Rightarrow P > P_0 \rightarrow$ damage the appliance.

$$V < V_0 \Rightarrow P < P_0$$

Long distance power transmission:

$$\text{Power loss} = I^2 R = P$$

also $P_0' = VI$

↳ given power

$$\Rightarrow I = \frac{P_0'}{V}$$

$$\Rightarrow \text{Power loss} = \frac{P_0'^2}{V^2} R$$

$$\Rightarrow \text{power loss} \propto \frac{1}{V^2}$$


more the potential drop, less the power loss.

OR say less the current, less the power loss.

So for given power P_0' , V should be high, I should be low

⇒ so transmission lines are high voltage power supplies


Appliance Combination

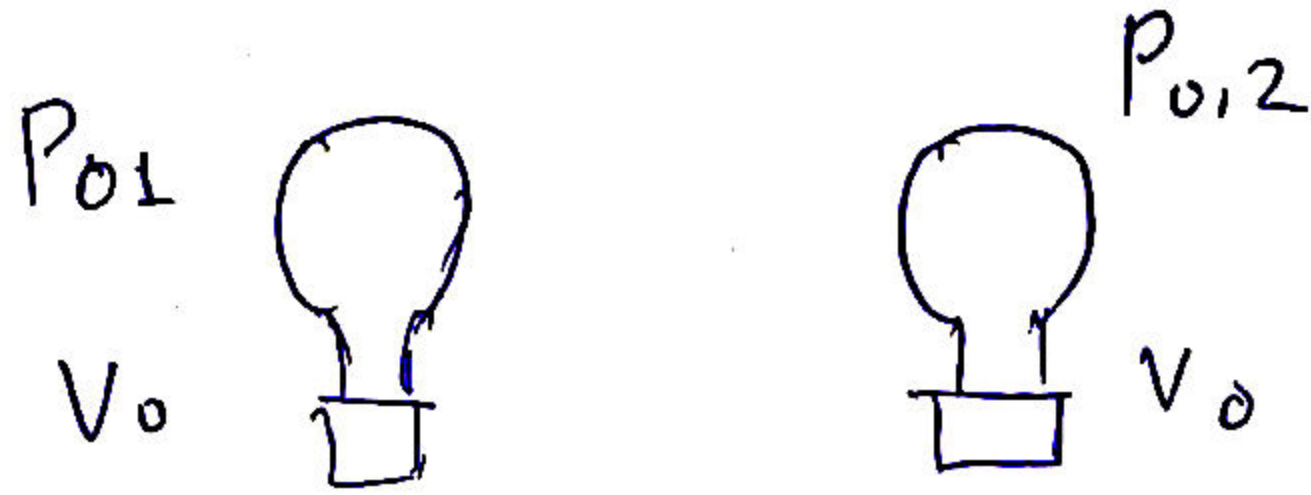

$$P_{01} > P_{0,2} \quad \left| \quad R_1 < R_2 \right.$$

$$\Rightarrow \frac{V_0^2}{R_1} > \frac{V_0^2}{R_2}$$

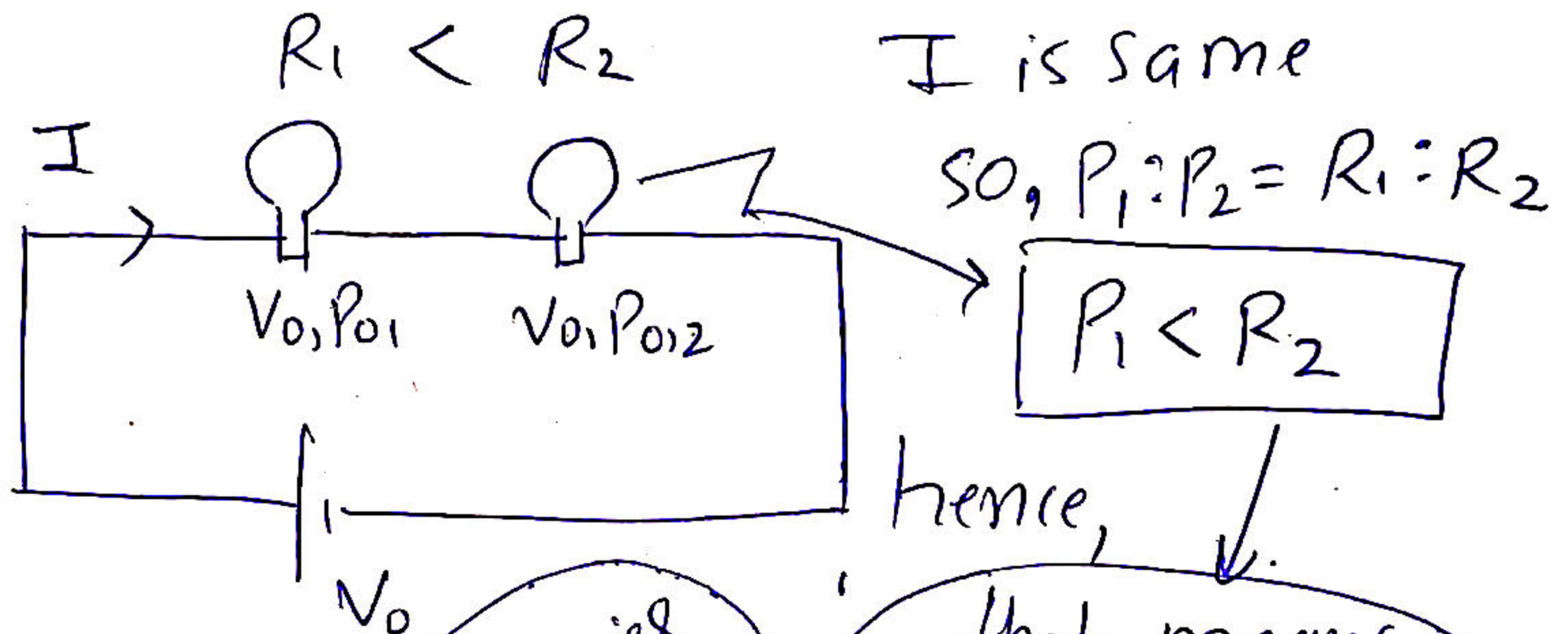higher power rating for same V_0 , means less Resistance.



$$I = \frac{V_0}{R_1 + R_2}$$

$$P_1 = I^2 R_1$$

$$P_2 = I^2 R_2$$

In series
low power rating glow brighter

hence, that means bulb 2 glow brighter

$$P_{net} = I^2 (R_1 + R_2) = P$$

total power consumed

$$P = \frac{V_0^2}{(R_1 + R_2)^2} (R_1 + R_2)$$

$$P = \frac{V_0^2}{(R_1 + R_2)}$$

$$\text{or } \frac{1}{P} = \frac{R_1 + R_2}{V_0^2} = \frac{R_1}{V_0^2} + \frac{R_2}{V_0^2}$$

$$\frac{1}{P} = \frac{1}{P_{01}} + \frac{1}{P_{02}}$$

$$\text{or } P = \frac{P_{01} \times P_{02}}{P_{01} + P_{02}}$$

only when applied voltage $V = V_0$

if $V \neq V_0$

$$P' = \left(\frac{V}{V_0}\right)^2 P$$

$$P' = \left(\frac{V}{V_0}\right)^2 \left[\frac{P_{01} \times P_{02}}{P_{01} + P_{02}} \right]$$


or In general

$$\frac{1}{P} = \frac{1}{P_{01}} + \frac{1}{P_{02}} + \dots + \frac{1}{P_{0n}}$$

Power consumed when $V = V_0$ → applied voltage

→ Rated voltage

$$P_{01} > P_{02}$$

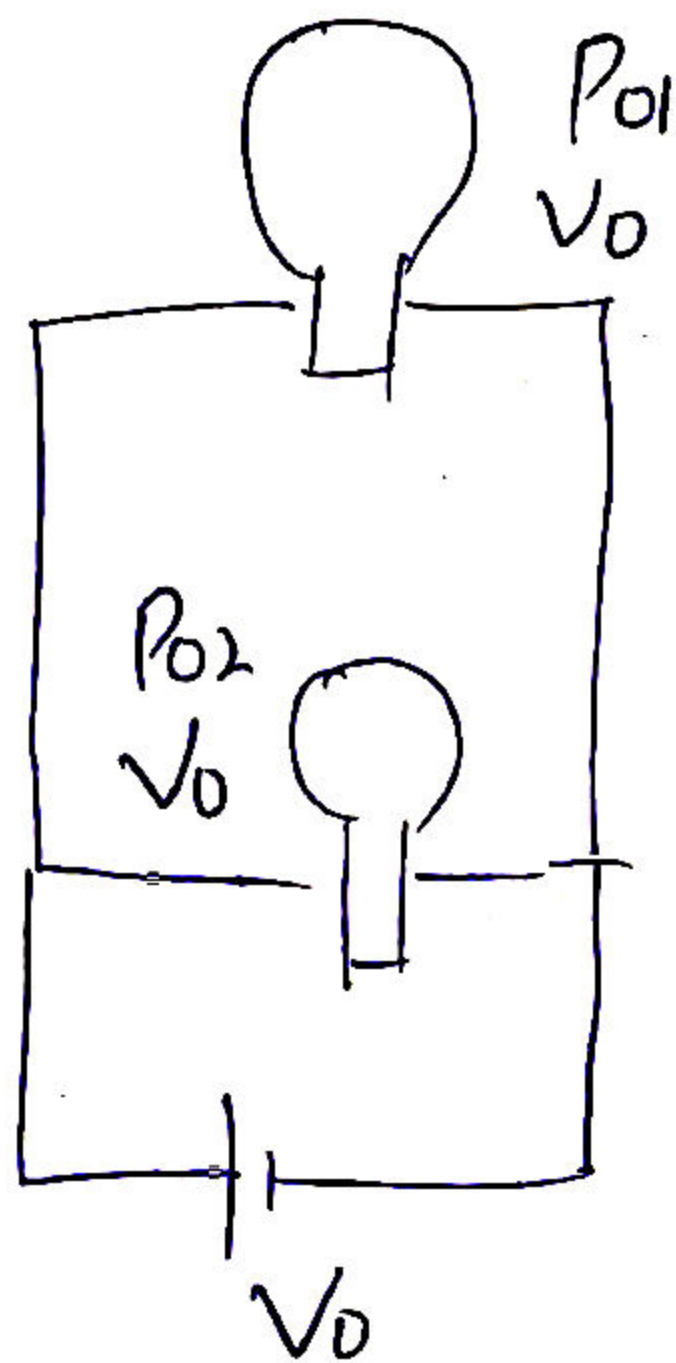

$R_1 < R_2 \Rightarrow$ for parallel

$$P_1 : P_2 = \frac{V^2}{R_1} : \frac{V^2}{R_2}$$

$$P_1 : P_2 = \frac{1}{R_1} : \frac{1}{R_2}$$

$$\Rightarrow P_1 > P_2$$

so 1 glow brighter in parallel

$$P_1 = \frac{V_0^2}{R_1} = P_{01}$$

$$P_2 = \frac{V_0^2}{R_2} = P_{02}$$

$$P = P_1 + P_2 = P_{01} + P_{02}$$

if $v = V_0$


if $v \neq V_0$

$$P' = \left(\frac{v}{V_0}\right)^2 P = \left(\frac{v}{V_0}\right)^2 [P_{01} + P_{02}]$$

in general \Rightarrow

$$P = P_1 + P_2 + \dots + P_n$$

Charging of Capacitor:

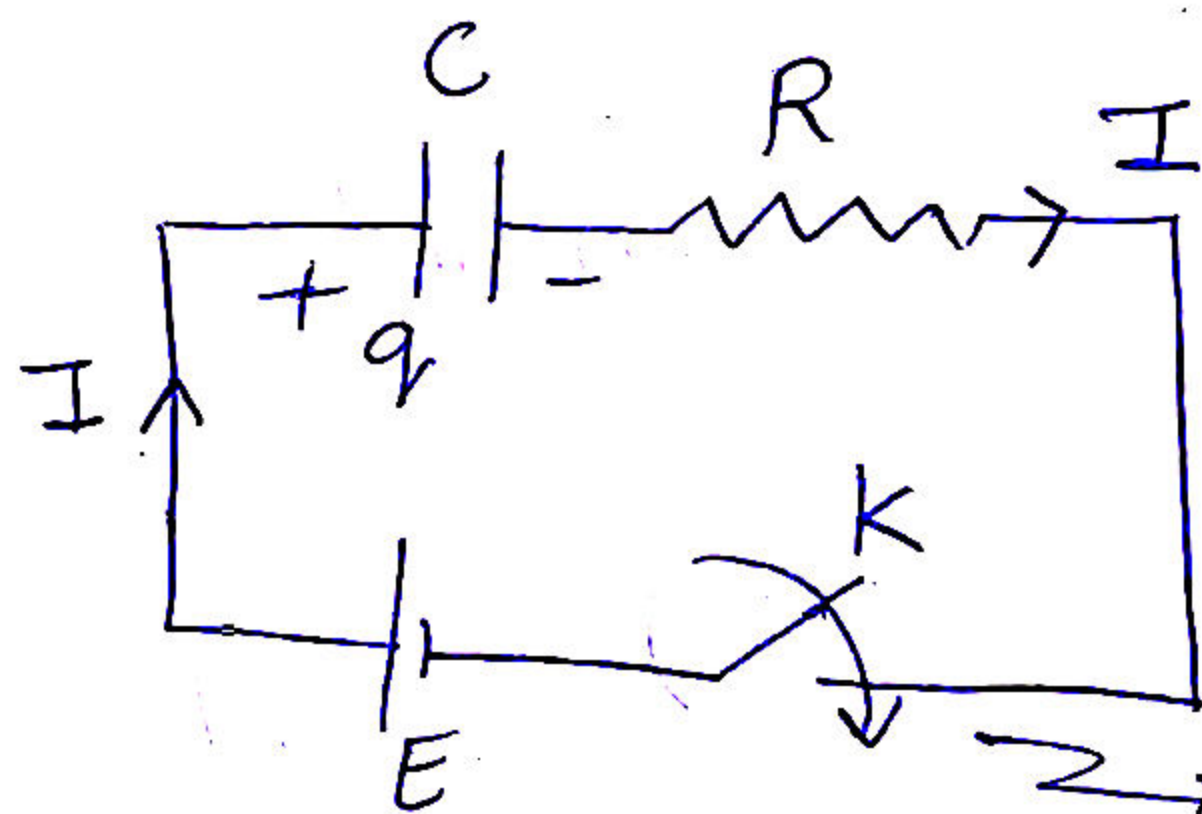

initial conditions:

$$t=0, q=0$$

$$I = \frac{dq}{dt}$$

key is closed

Applying kirchhoff's law

$$E = \frac{q}{C} + IR$$

$$E = \frac{q}{C} + \frac{dq}{dt}R$$

$$\Rightarrow \int R \frac{dq}{dt} = \int \frac{-q}{C} + E$$

$$\Rightarrow \int_0^{q_0} \frac{dq}{(EC - q)} = \int_0^t \frac{dt}{RC}$$

$$\ln(EC - q) = \ln EC - \frac{t}{RC}$$

$$\ln \left[\frac{EC - q}{EC} \right] = -\frac{t}{RC}$$

$$\frac{EC - q}{EC} = e^{-t/RC}$$

$$q = EC [1 - e^{-t/RC}]$$


$\tau = RC \rightarrow$ time constant

When $t = \tau$

$$q = Q (1 - e^{-\tau/\tau}) = Q (1 - e^{-1})$$

$$q = 0.632Q$$

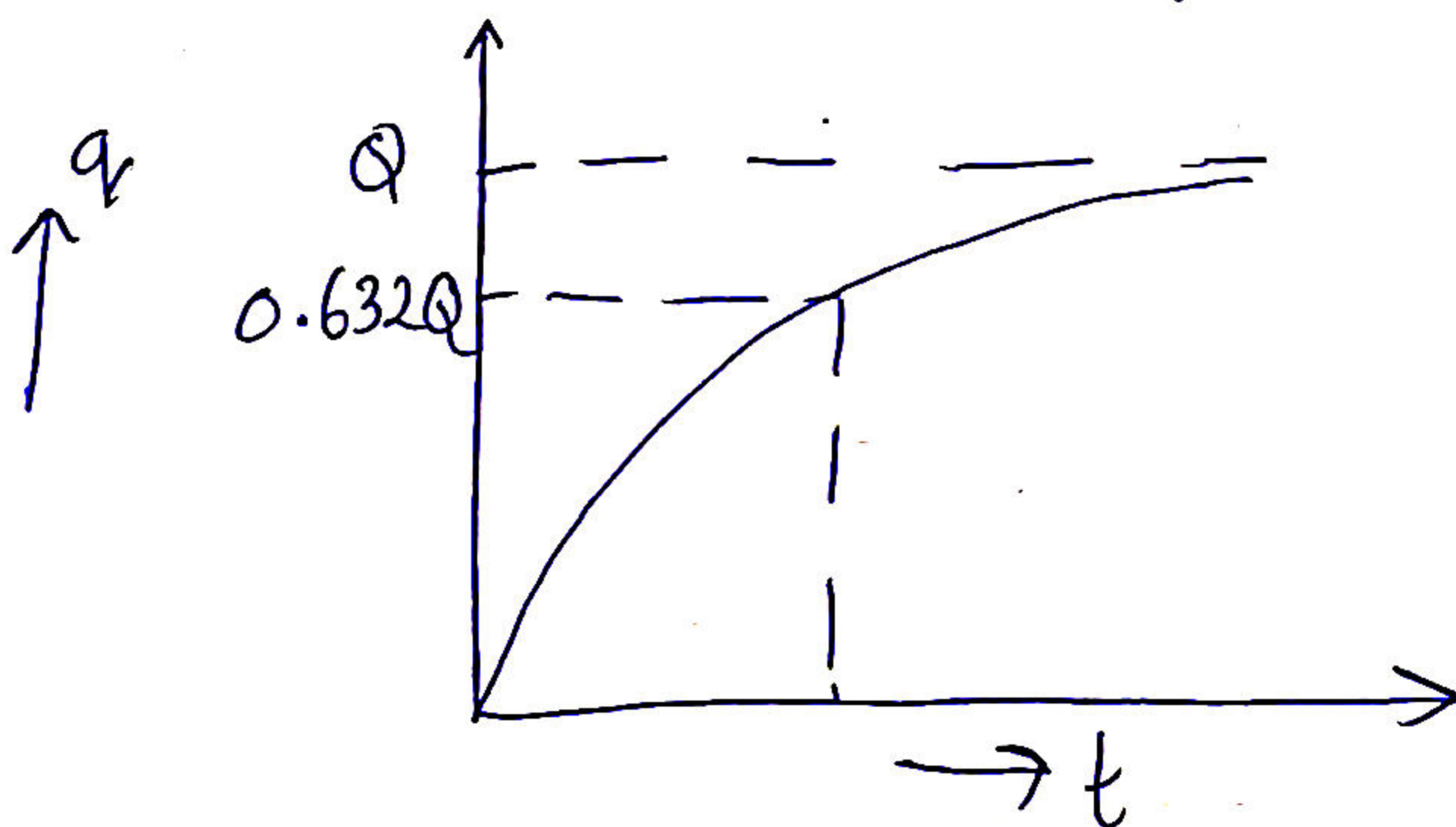So, $t \rightarrow \tau$, charging to 63.2%




$$I = \frac{dq}{dt} = Q \left[0 - e^{-t/\tau} \left(-\frac{1}{\tau} \right) \right]$$


$$I = \frac{Q}{\tau} e^{-t/\tau} \Rightarrow \boxed{I = \frac{EC}{RC} e^{-t/\tau}}$$

$$\boxed{I = I_0 e^{-t/\tau}}$$

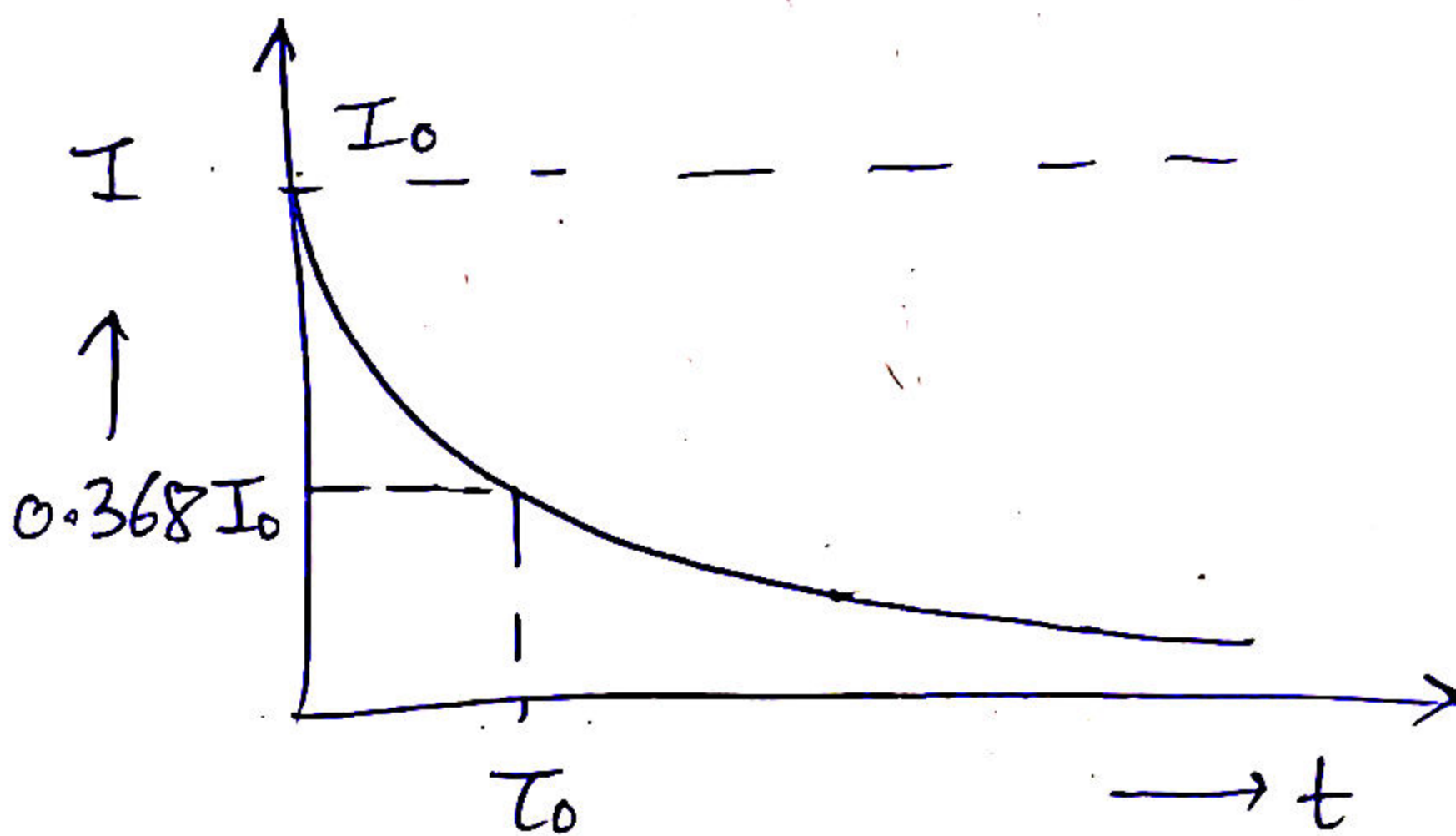When $t \rightarrow \tau \Rightarrow \boxed{I = \frac{I_0}{e} = 0.368 I_0}$



DISCHARGING OF CAPACITOR:

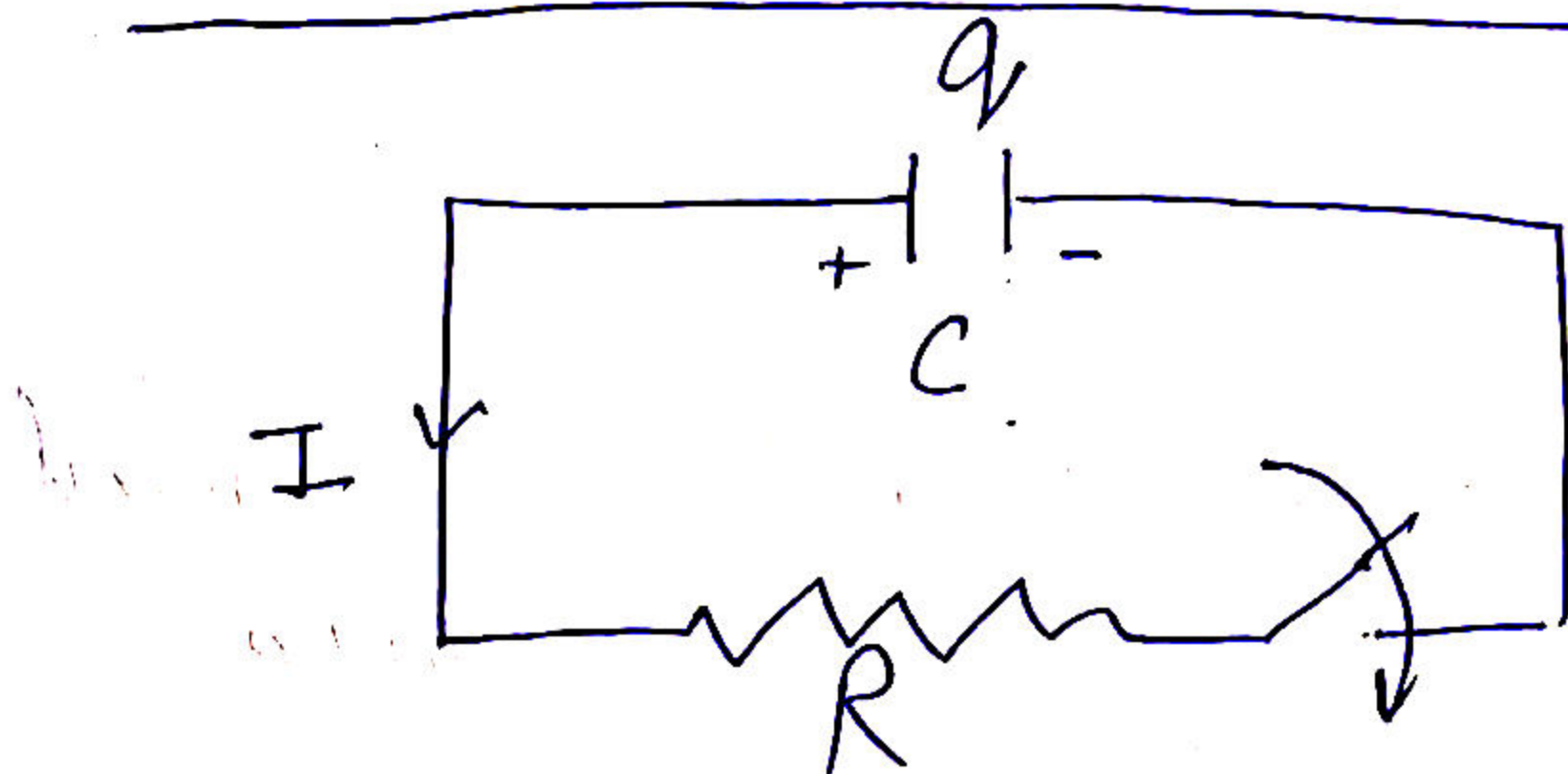

At $t=0$,
 $q = Q \Rightarrow$ initial charge
 $I = \frac{-dq}{dt}$

Applying kirchhoff's law:

$$\frac{q}{c} = IR \Rightarrow \frac{q}{c} = -\frac{dq}{dt} R$$

$$\int_Q^q \frac{dq}{q} = -\int_0^t \frac{dt}{RC}$$

$$\Rightarrow \ln\left(\frac{q}{Q}\right) = -t/RC$$

$$\Rightarrow \boxed{q = Q e^{-t/RC}}$$

$$RC = \tau$$

When

$$\boxed{t = \tau}$$


$$\Rightarrow \boxed{q_1 = Q e^{-t/\tau}}$$

$$\Rightarrow q_1 = Q e^{-\tau/\tau}$$

$$\boxed{q_1 = Q e^{-1} = \frac{Q}{e}}$$

$$\Rightarrow \boxed{q_1 = 0.368Q}$$

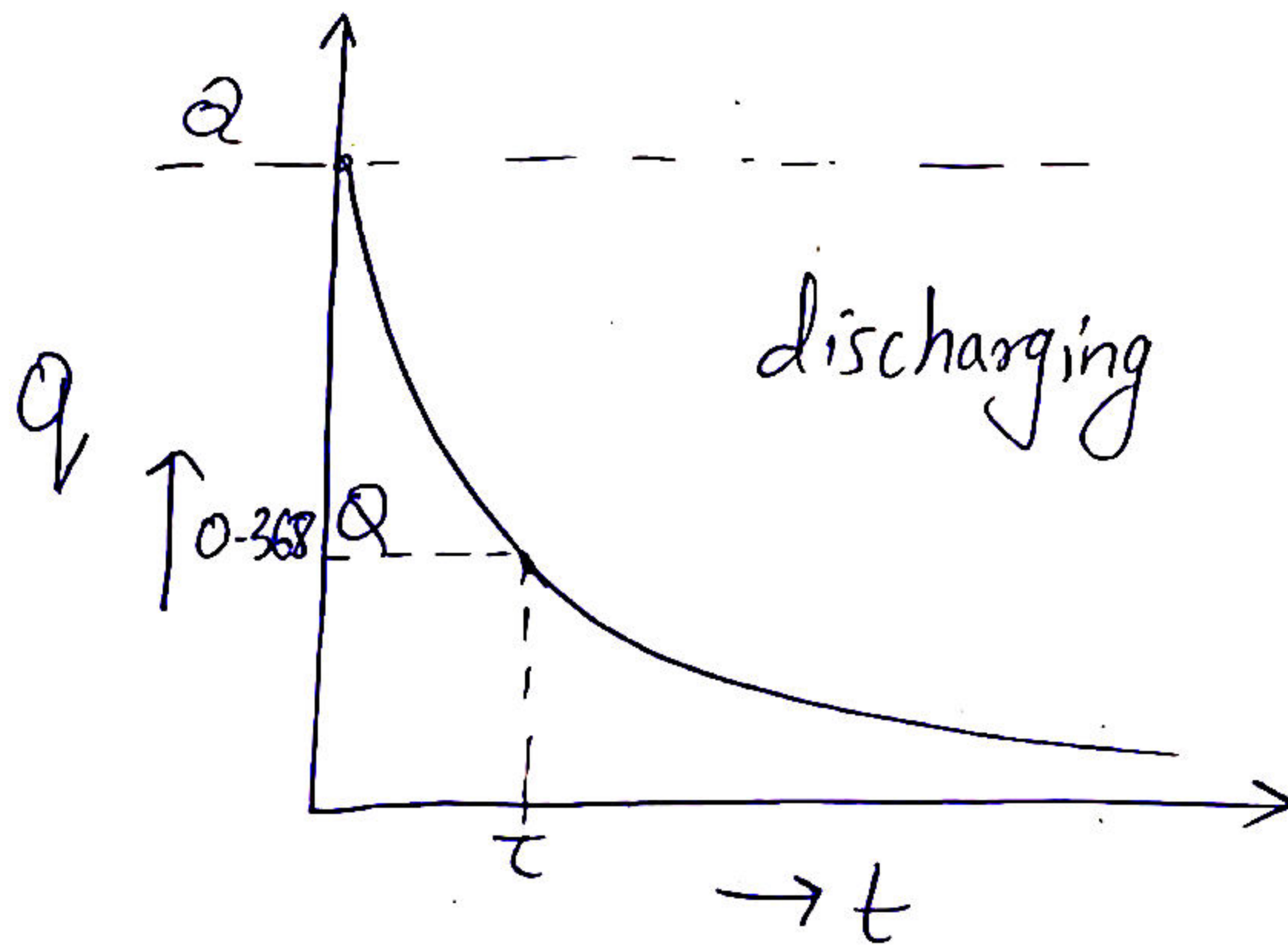So $t \rightarrow \tau$, $q \rightarrow 36.8\%$ of initial charge



Energy considerations in charging:

Total work done by battery in fully charging the capacitor

$$W_b = EQ = E^2 C \quad [\text{as } Q = EC]$$

$$U = \frac{1}{2} CE^2$$

↳ emf of battery

as $I \neq 0$ $H = \int_0^{\infty} I^2 R dt = \int_0^{\infty} I_0^2 e^{-2t/\tau} R dt$

Heat dissipated in resistor

$$= I_0^2 R \left[\frac{e^{-2t/\tau}}{-2\tau} \right]_0^{\infty}$$

$$H = \frac{-I_0^2 R \tau (0 - 1)}{2}$$

so, total $W_b = CE^2$

one half
dissipated in heat

$$H = \frac{1}{2} CE^2$$

Energy consideration in discharging:

energy loss, $H = \int_0^{\infty} I^2 R dt$

$$\Rightarrow H = \int_0^{\infty} \left(\frac{Q}{RC} \right)^2 e^{-2t/\tau} R dt$$


$$H = \frac{-Q^2 RC [0-1]}{2RC^2}$$

$$H = \frac{1}{2} \frac{Q^2}{C}$$

initial energy stored in capacitor


So whole energy is dissipated in form of heat.

Equivalent Time Constant

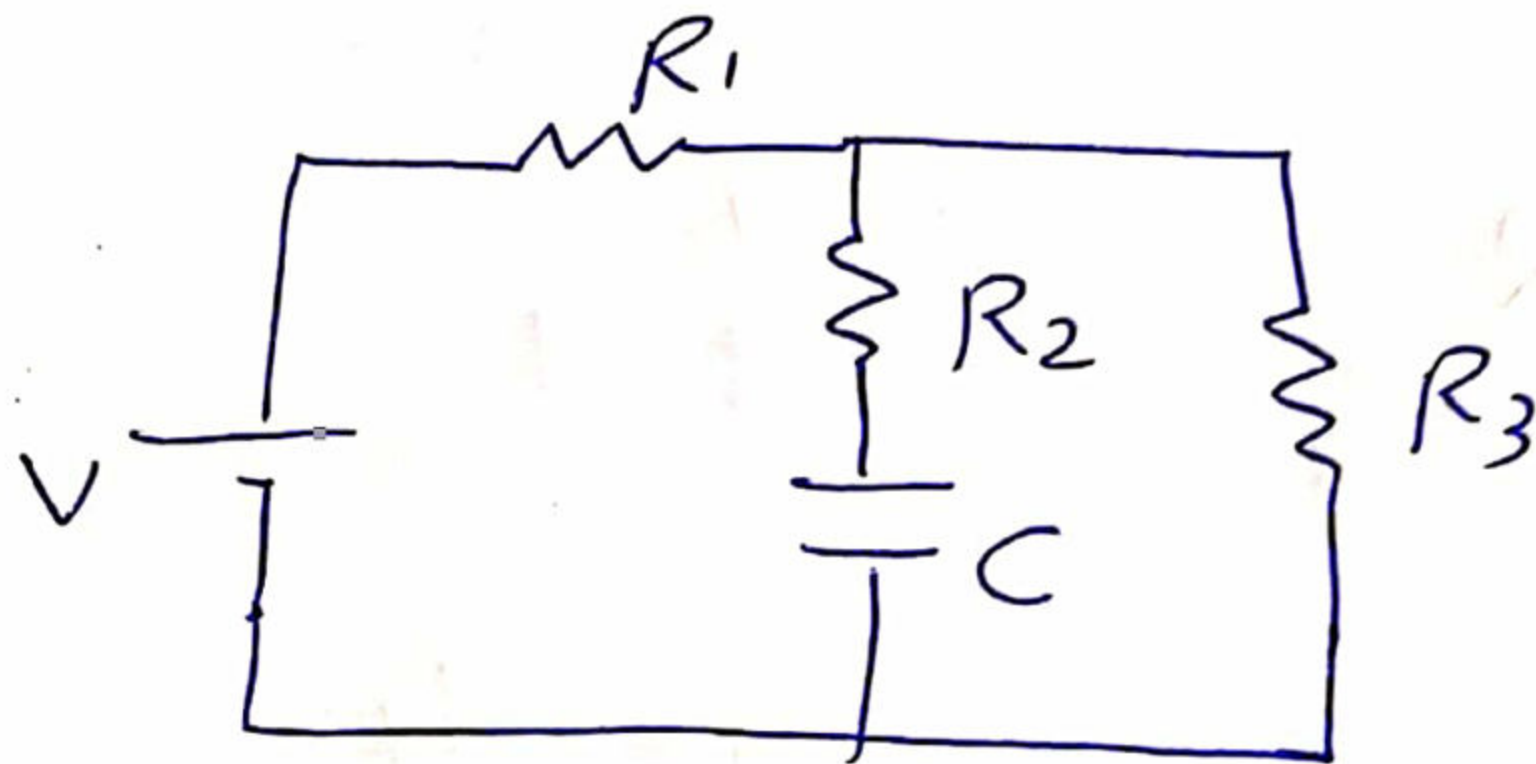

$$\tau_{eq} = (R_{eq}) C$$

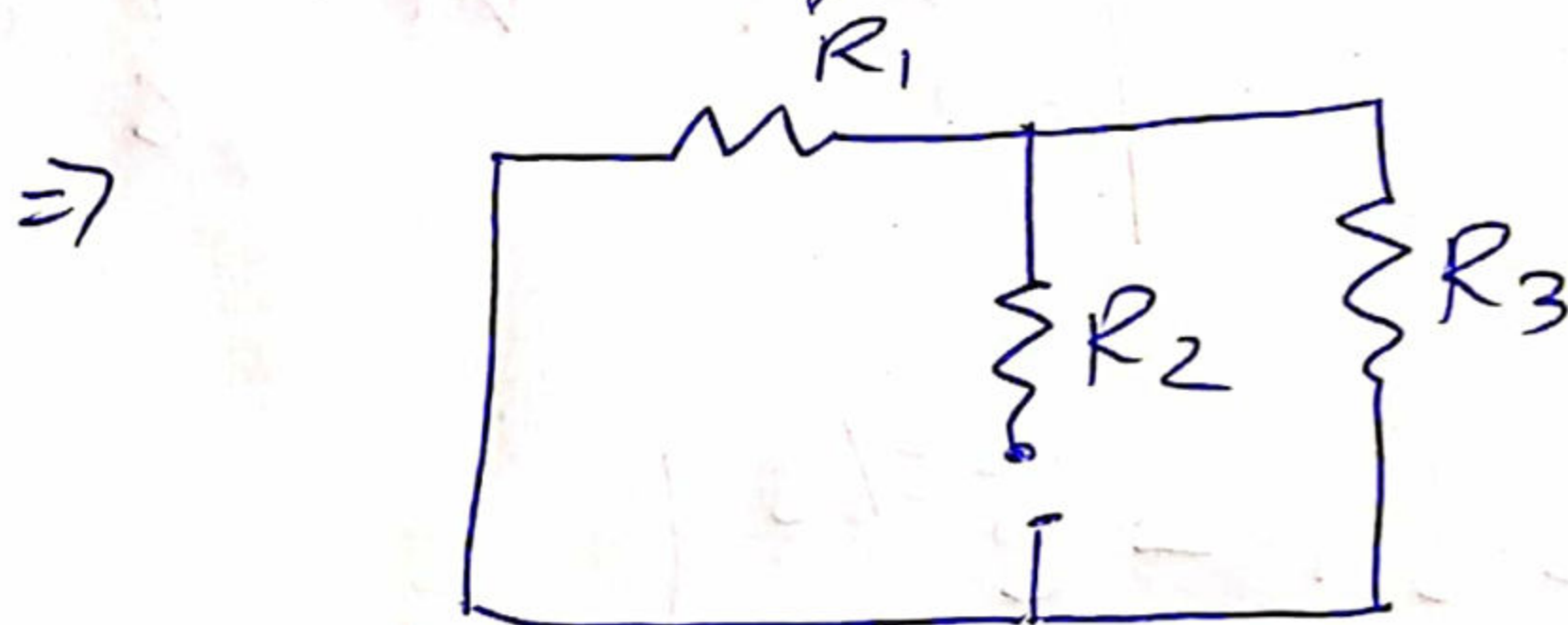replace battery by short-circuit
and capacitor by open circuit
and find R_{eq} around C




\Rightarrow

$$R_{eq} = \frac{R_1 \cdot R_3}{R_1 + R_3} + R_2$$

So

$$\tau_{eq} = R_{eq} C$$

for charging RC circuit:

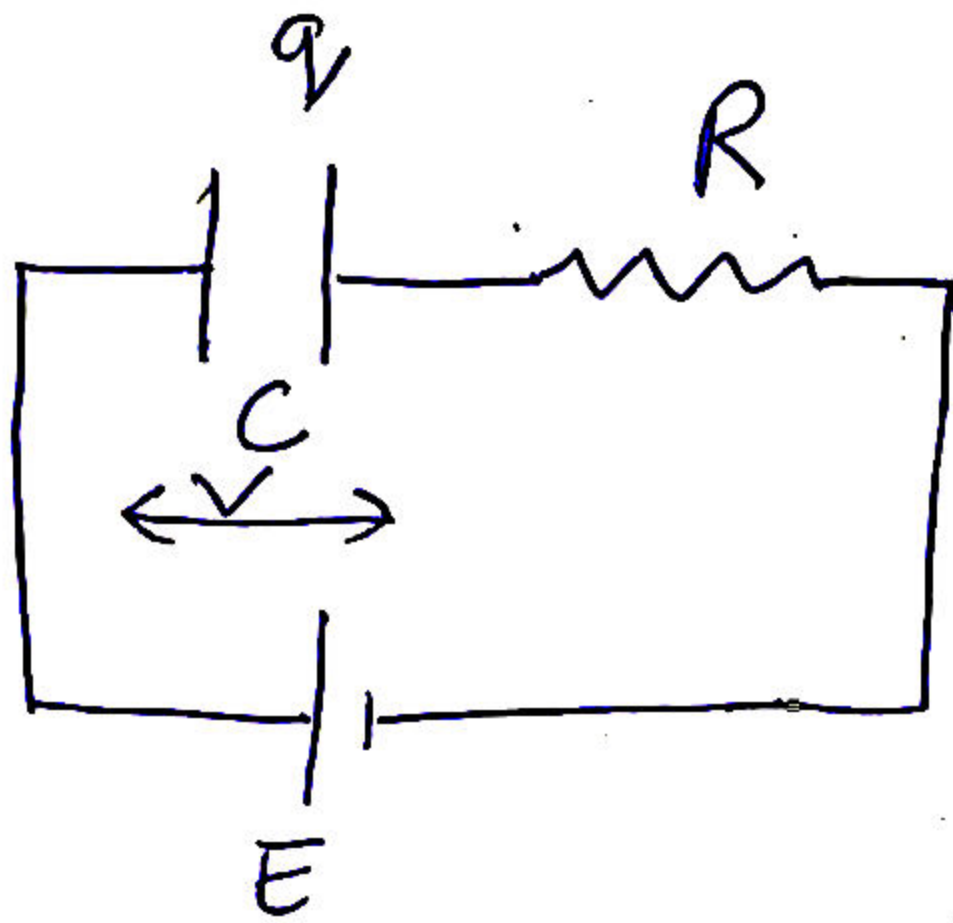

$$V = \frac{q}{C}$$

$$P_c = \frac{dU_c}{dt}$$

Power transferred to capacitor

$$\Rightarrow P_c = V i = \frac{q}{C} i$$

$$q = Q [1 - e^{-t/\tau}]$$

$$Q = EC$$


$$\Rightarrow i = \frac{E}{R} e^{-t/\tau}$$

$$P_c = \frac{EC [1 - e^{-t/\tau}]}{C} \frac{E}{R} e^{-t/\tau}$$

$$P_c = \frac{E^2}{R} [1 - e^{-t/\tau}] e^{-t/\tau}$$

$P_B \rightarrow$ power delivered by battery
 $= E i^a$

$$P_B = \frac{E^2}{R} e^{-t/\tau}$$

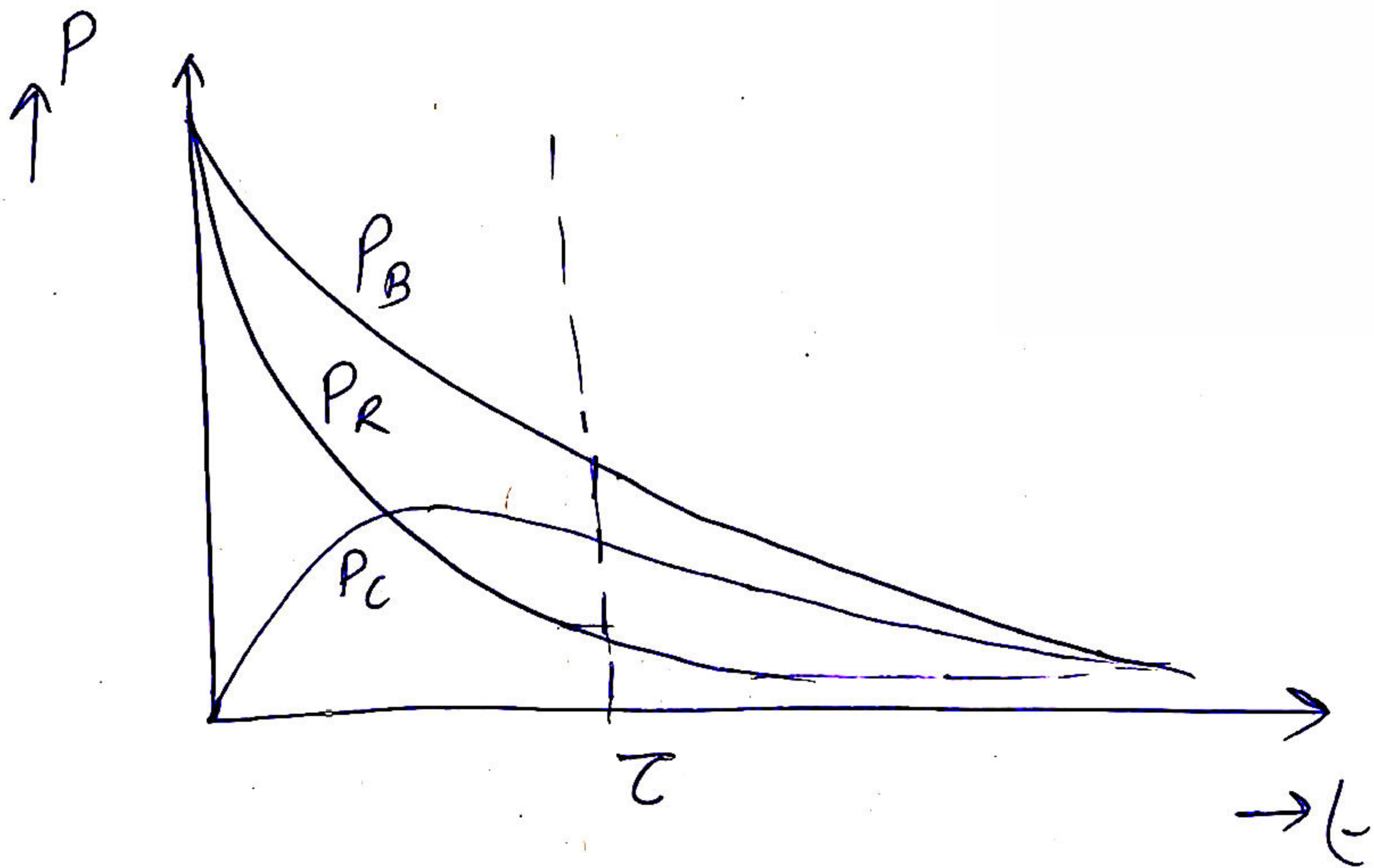

$$P_R = i^2 R = \left[\frac{E}{R} e^{-t/\tau} \right]^2 R$$

\hookrightarrow power dissipated by resistor

$P_C \neq P_R$ at any time t'

\Rightarrow But $P_R + P_C = P_B$

$P_c \rightarrow \text{max}$

$$\frac{dP_c}{dt} = 0$$


$$\frac{d}{dt} \left[\frac{E^2}{R} (e^{-t/\tau} - e^{-2t/\tau}) \right] = 0$$

$$e^{-t/\tau} \left[\frac{1}{\tau} \right] - e^{-2t/\tau} \left[\frac{2}{\tau} \right] = 0$$

$$\Rightarrow e^{t/\tau} = 2$$

$$\text{or } \boxed{t = \tau \ln 2}$$

For discharging RC circuit:

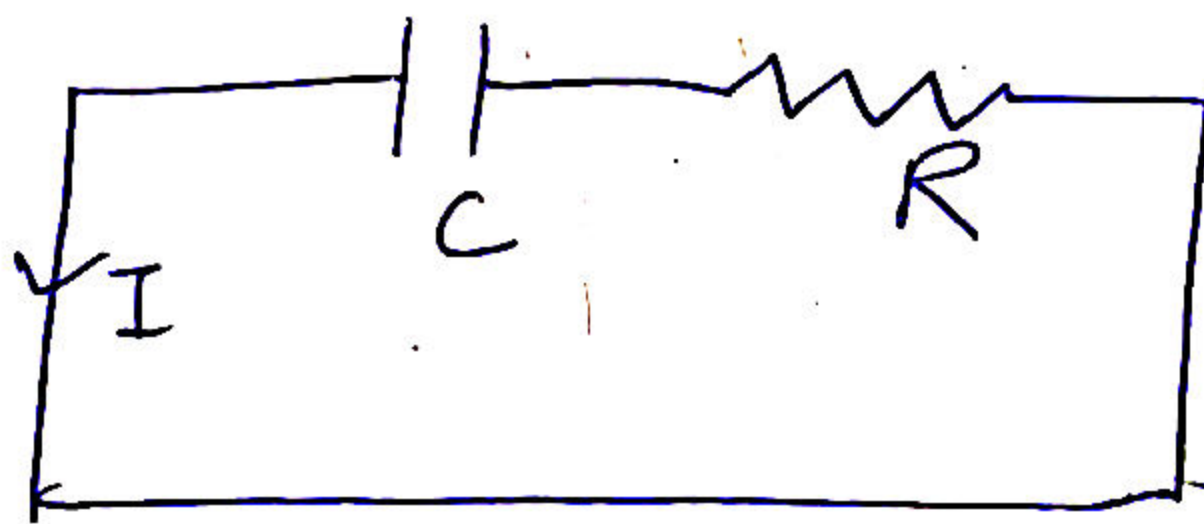

$$q = Q e^{-t/\tau}$$

$$i = i_0 e^{-t/\tau}$$

$$\boxed{q = EC e^{-t/\tau}}$$

$$\boxed{Q = EC}$$

$$\boxed{i = \frac{E}{R} e^{-t/\tau}}$$

$P_c = \frac{dU}{dt}$ rate at which energy is transferred

$$\begin{aligned}
 P_C &= \frac{dU}{dt} = \frac{d}{dt} \left[\frac{q^2}{2C} \right] \\
 &= \frac{d}{dt} \left[\frac{E^2 C^2}{2C} e^{-2t/\tau} \right] \\
 &= \frac{E^2 C}{2} \left[e^{-2t/\tau} \left[-\frac{2}{\tau} \right] \right]
 \end{aligned}$$

$$P_C = -\frac{E^2}{R} e^{-2t/\tau}$$

P_R = energy dissipation by resistor

$$\begin{aligned}
 P_R &= I^2 R \\
 &= \frac{E^2}{R^2} e^{-2t/\tau} R
 \end{aligned}$$

$$P_R = \frac{E^2}{R} e^{-2t/\tau}$$

\Rightarrow $P_C = -P_R$

\swarrow energy dissipated by capacitor will be lost by resistor.

\searrow or rate of energy decrease in capacitor

